

Matrix Classes

Day-1

JEE Main


Physics-CCJMP01

Assignment-Logic Gates, PN Junction Diode and Zener Diode

Logic Gates


Straight Objective

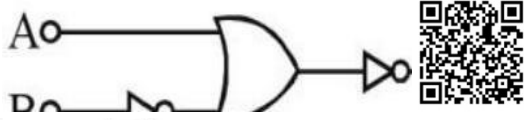Q 1. The logic circuit shown above is equivalent to :




- (a) (b)
- (c) (d)

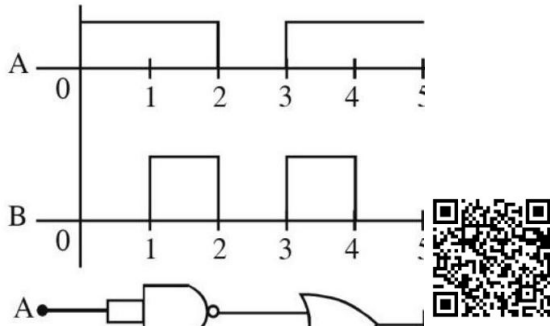Q 2. Draw the output signal **Y** in the given combination of gates :-




- (a) (b)
- (c) (d)

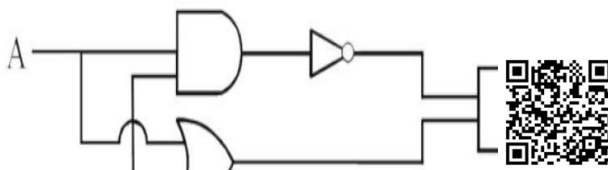Q 3. Which one of the following will be the output of the given circuit?




- (a) NOR Gate (b) NAND Gate
- (c) AND Gate (d) XOR Gate

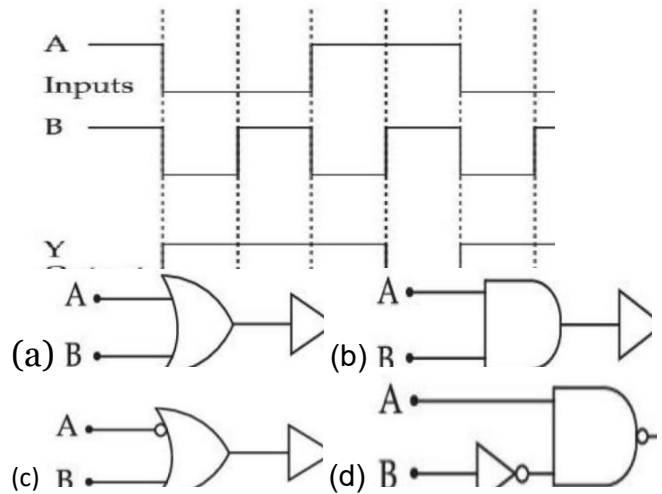Q 4. Identify the correct Logic Gate for the following output (Y) of two inputs A and B.




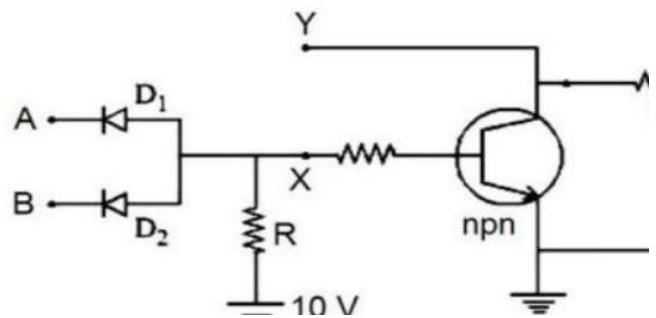
Q 5. In the following circuit, the correct relation between output (**Y**) and inputs **A** and **B** will be :



- (a) $Y = AB$ (b) $Y = A + B$
- (c) $Y = \overline{AB}$ (d) $Y = \overline{A + B}$

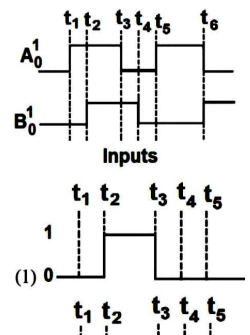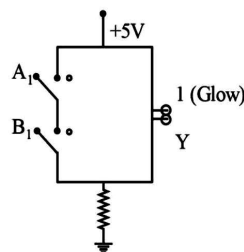
Q 6. The logic gate equivalent to the given circuit diagram is :

Logic gate equivalent to the given circuit diagram is :




- (a) OR (b) NOR (c) NAND (d) AND

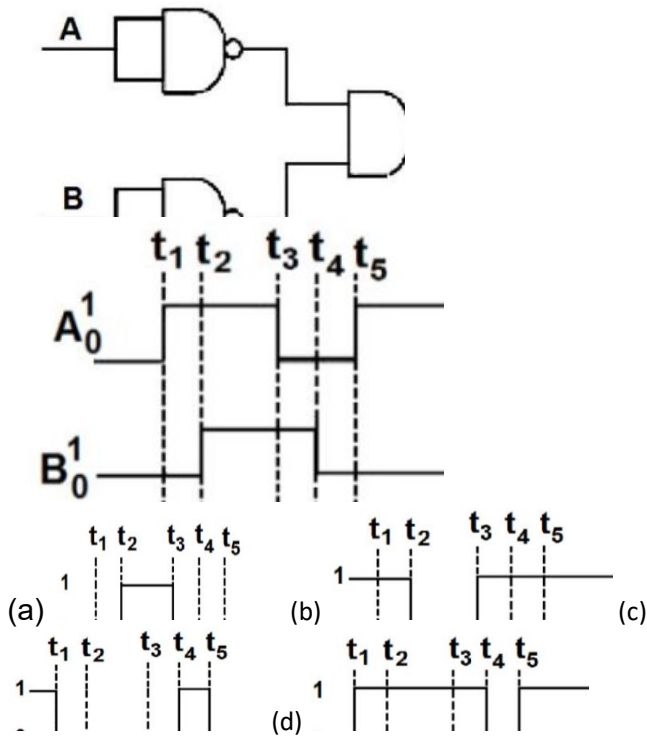Q 7. The output waveform of the given logical circuit for the following inputs A and B as shown below, is :



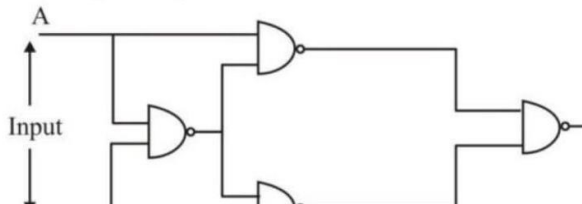Q 8. The output Y for the inputs A and B of circuit is given by



Truth table of the shown circuit is :

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

(a)

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

(b)


A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

(c)

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	0


(d)

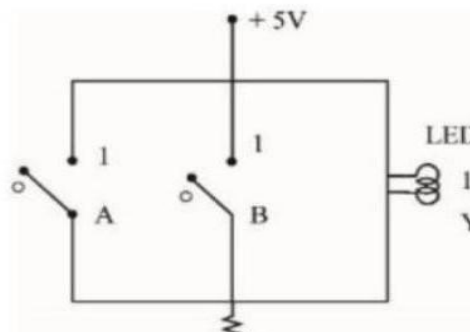Q 9. Name the logic gate equivalent to the diagram attached




(a) OR (b) NOR (c) NAND (d) AND

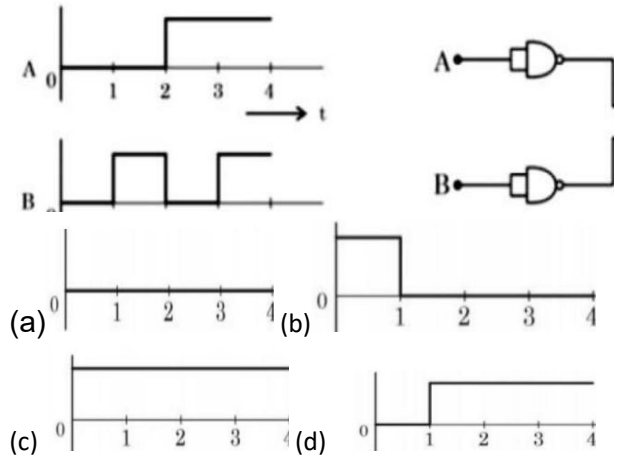Q 10. For the logic circuit shown, the output waveform at Y is:



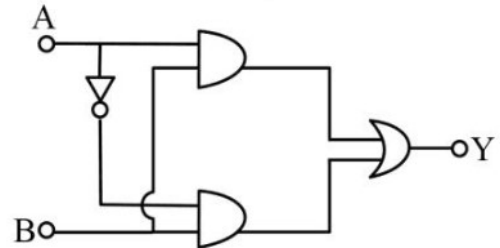Q 11. The truth table for this given circuit is :



A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

(a)

A	B	Y
0	0	0
0	1	1
1	0	0
1	1	1

(b)


A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

(c)

A	B	Y
0	0	1
0	1	0
1	0	1
1	1	0


(d)

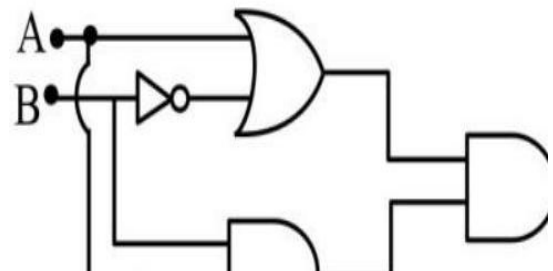Q 12. The output Y of following circuit for given inputs is :




(a) $A \cdot B(A + B)$ (b) $A \cdot B$
 (c) 0 (d) $\bar{A} \cdot B$

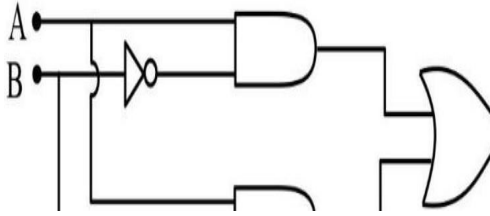Q 13. Which of the following circuits has the same output as that of the given circuit?



- (a) (2) (b) (c) (d)

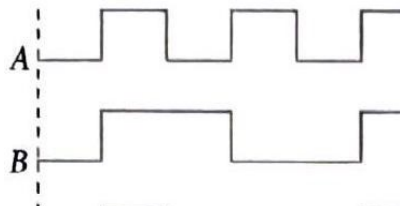Q 14. A logic gate circuit has two inputs **A** and **B** and output **Y**. The voltage waveforms of **A**, **B** and **Y** are shown below. The logic gate circuit is



- (a) AND gate (b) OR gate
(c) NOR gate (d) NAND gate

Q 15. The output of a 'NAND' gate is shown in the truth-table (**A** and **B** are inputs, **Y** is output)

P)

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

Q)

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

R)


A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

S)

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0


- (a) P (b) R (c) Q (d) S

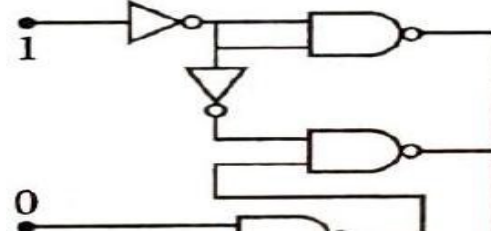Q 16. In the given circuit, value of **Y** is




- (a) toggles between 0 and 1 (b) 1
(c) 0 (d) will not execute.

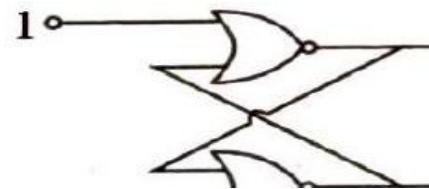Q 17. In the following circuit, what are **P** and **Q** ?



- (a) $P = 0, Q = 1$ (b) $P = 0, Q = 0$
(c) $P = 1, Q = 1$ (d) $P = 1, Q = 0$

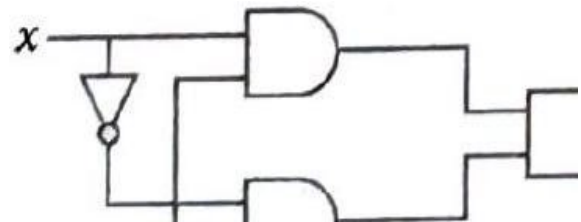Q 18. Truth table for the following digital circuit will be



- (a)

x	y	z
0	0	1
0	1	1
1	0	1
1	1	1

 (b)

x	y	z
0	0	0
0	1	0
1	0	0
1	1	1


- (c)

x	y	z
0	0	0
0	1	1
1	0	1
1	1	1

 (d)


x	y	z
0	0	1
0	1	1
1	0	1
1	1	0

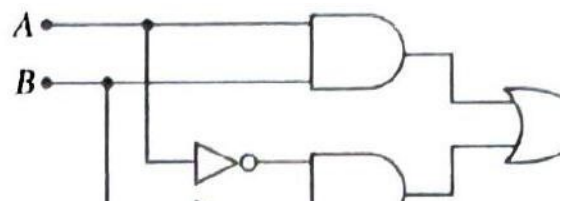Q 19. In the given circuit, the binary inputs at **A** and **B** are both 1 in one case and both 0 in the next case. The respective outputs at **Y** in these two cases will be




- (a) 1,1 (b) 0,0 (c) 0,1 (d) 1,0

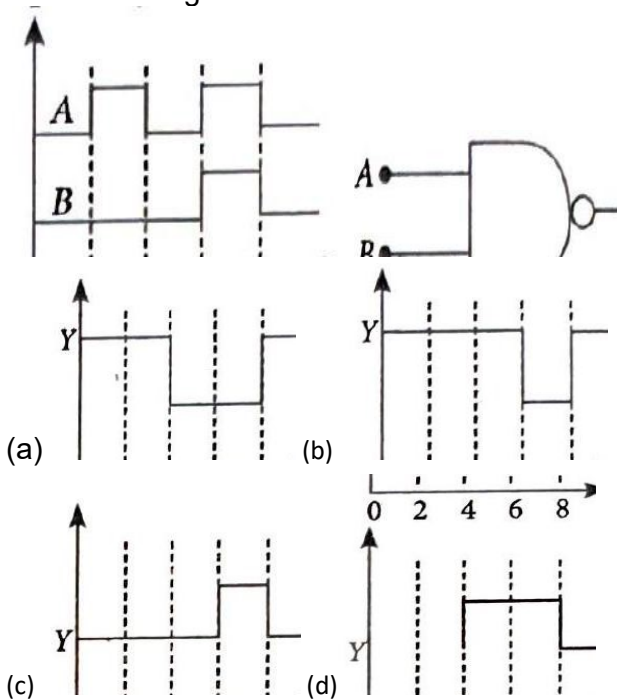Q 20. The real time variation of input signals A and B are as shown in the figure. If the inputs are fed into NAND gate, then select the output signal from the following.




Integer type Questions

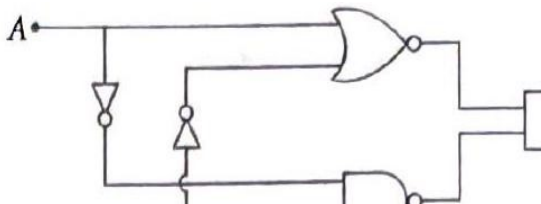
Q 21. In the logic circuit shown in the figure, if input A and B are 0 to 1 respectively, the output at Y would be 'x'. The value of x is ____.



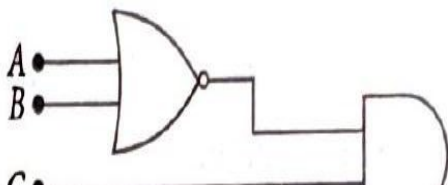Q 22. A NOR gate and a NAND gate are connected as shown in the figure. Two different sets of inputs are given to this set up. In the first case, the inputs to the gates are $A = 0, B = 0, C = 0$. In the second case, the inputs are $A = 1, B = 0, C = 1$. The output D in the second case is ____.




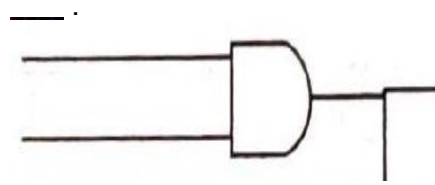Q 23. The output Y , when all the three inputs are first high will be



Q 24. The value $(\bar{1} + \bar{1}) \cdot (\bar{0} + 0)$ of is ____.

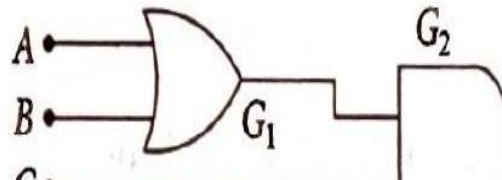
Q 25. For the given combination of gates, if the logic states of inputs A, B, C are as follows $A = B = C = 0$ and $A = B = 1, C = 0$, then the logic states of output D are ____.




Zener Diode

Straight Objective

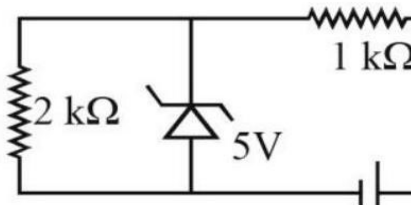
Q 26. In connection with the circuit drawn below, the value of current flowing through $2\text{k}\Omega$ resistor is $x \times 10^{-4}$ A.



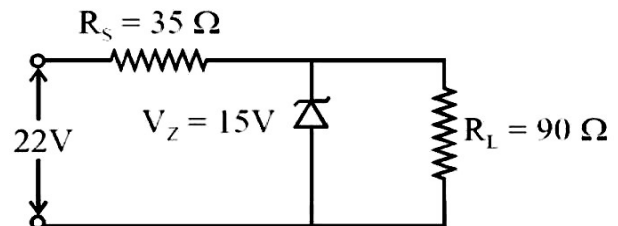
Q 27. The value of power dissipated across the Zener diode ($V_z = 15\text{ V}$) connected in the circuit as shown in the figure is $x \times 10^{-1}$ watt. The value of x , to the nearest integer, is



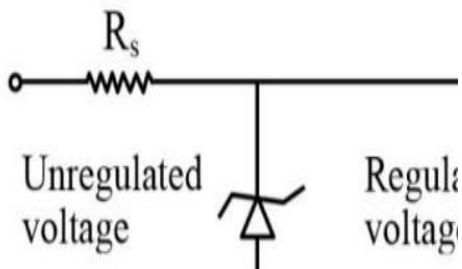Q 28. A Zener diode of power rating 2 W is to be used as a voltage regulator. If the Zener diode has a breakdown of 10 V and it has to regulate voltage fluctuated between 6 V and 14 V , the value of R_s for safe operation should be Ω .




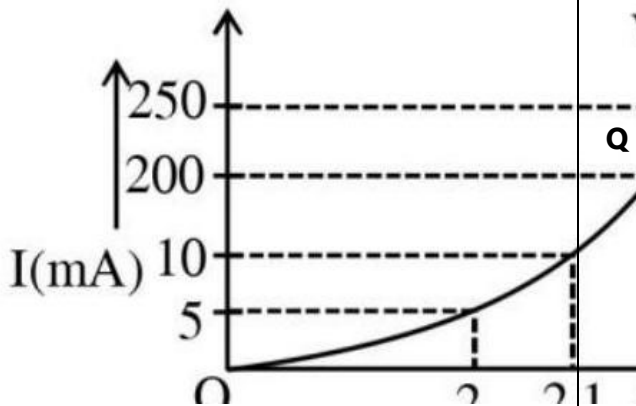Q 29. The I-V characteristics of a p-n junction diode in forward bias is shown in the figure. The ratio of dynamic resistance, corresponding to forward bias voltages of 2 V and 4 V respectively, is :




- (a) 1:2 (b) 1:40 (c) 5:1 (d) 20:1

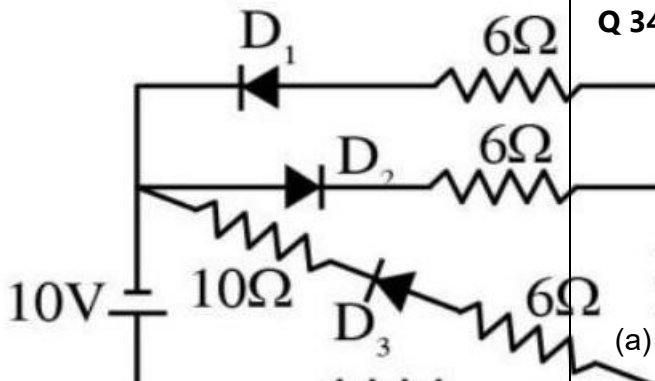
Q 30. As per the given circuit, the value of current through the battery will be A.



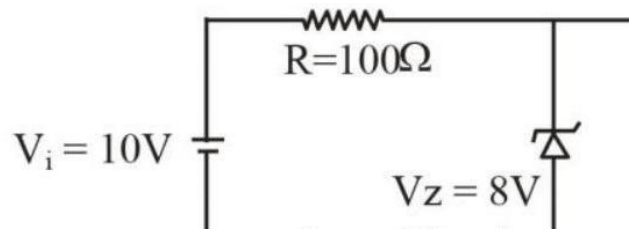
Q 31. A Zener of breakdown voltage $V_Z = 8\text{ V}$ and maximum Zener current, $I_{ZM} = 10\text{ mA}$ is subjected to an input voltage $V_i = 10\text{ V}$ with series resistance $R = 100\Omega$. In the given circuit R_L represents the variable load resistance. The ratio of maximum and minimum value of R_L is



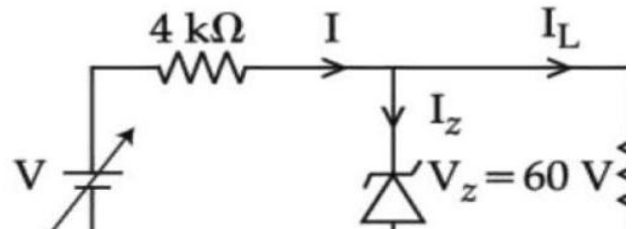Q 32. In the circuit shown below, maximum Zener diode current will be **mA** ($V = 100 - 120\text{ volt}$)




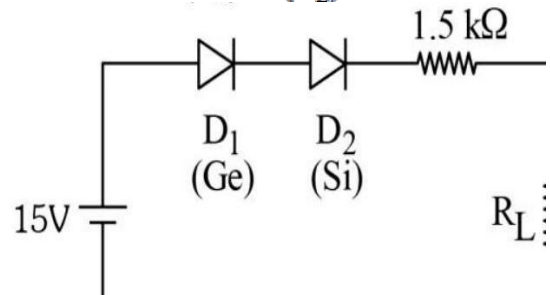Q 33. In the given circuit, the voltage across load resistance (R_L) is:




- (a) 8.75 V (b) 9.00 V
(c) 8.50 V (d) 14.00 V

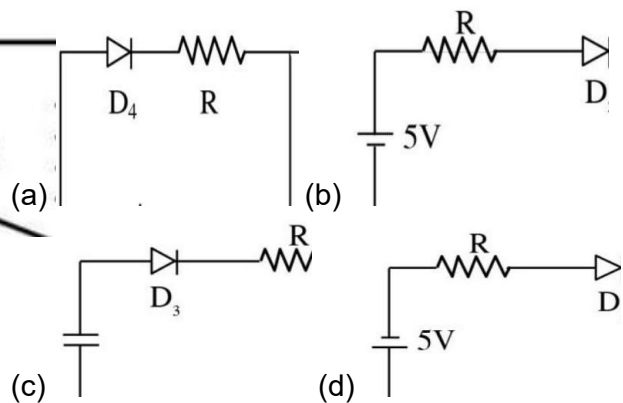Q 34. Which of the diode circuit shows correct biasing used for the measurement of dynamic resistance of p-n junction diode :




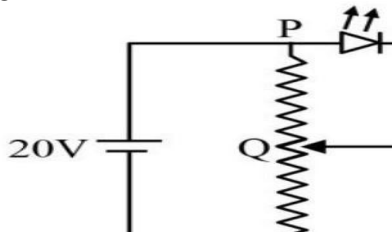Q 35. A potential divider circuit is connected with a dc source of 20 V, a light emitting diode of glow in voltage 1.8 V and a Zener diode of breakdown voltage of 3.2 V. The length (PR) of the resistive wire is

20 cm . The minimum length of PQ to just glow the LED is cm .




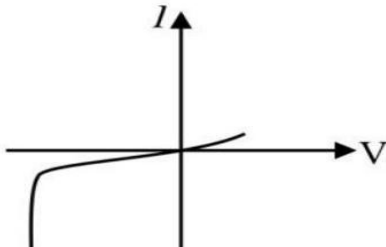Q 36. The $I - V$ characteristics of an electronic device shown in the figure. The device is :




- (a) a solar cell
- (b) a transistor which can be used as an amplifier
- (c) a Zener diode which can be used as voltage regulator
- (d) a diode which can be used as a rectifier

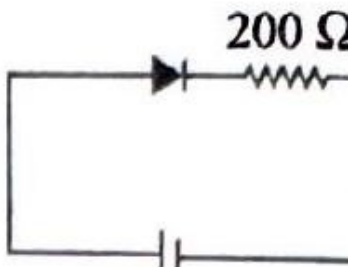Q 37. The reading of the ammeter for a silicon diode in the given circuit is




- (a) zero (b) 15 mA (c) 11.5 mA (d) 13.5 mA

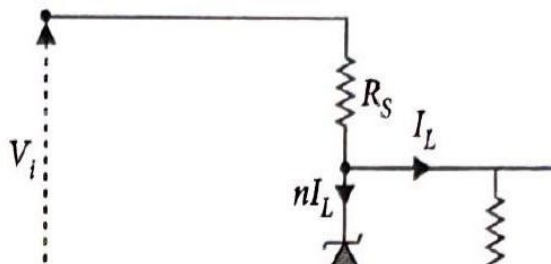Q 38. The value of the resistor, R_S , needed in the dc voltage regulator circuit shown here, equals



- (a) $(V_i - V_L)/nI_L$ (b) $(V_i + V_L)/nI_L$
- (c) $(V_i - V_L)/(n + 1)I_L$ (d) $(V_i + V_L)/(n + 1)I_L$

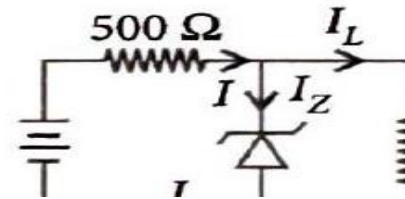
Q 39. In the circuit shown below if the current through the 500Ω resistor is 25 mA and that through the load R_L is 5 mA , then the maximum current through the Zener



diode is

- (a) 5 mA (b) 20 mA
- (c) 30 mA (d) 125 mA

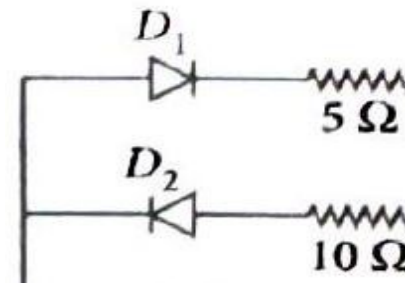
Q 40. A 2 V battery is connected across AB as shown in the figure. The value of the current supplied by the battery when in one case battery's positive terminal is connected to A and in other case when positive terminal of battery is connected to B will respectively be



- (a) 0.2 A and 0.1 A (b) 0.4 A and 0.2 A
- (c) 0.1 A and 0.2 A (d) 0.2 A and 0.4 A


Integer type Questions

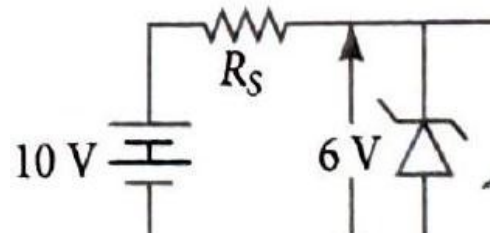Q 41. A Zener diode having break down voltage $V_z = 6 V$ is used in a voltage regulator circuit as shown in the figure. The minimum current required to pass through the Zener to act as a voltage regulator is 10 mA and maximum allowed current through Zener is 40 mA . The maximum value of R_S (in Ω) for Zener to act as a voltage regulator is ____ .




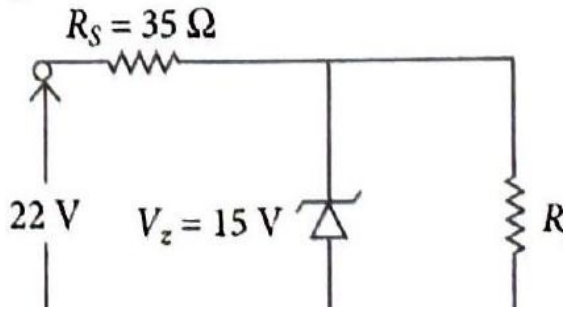Q 42. The value of power dissipated across the Zener diode ($V_z = 15 V$) connected in the circuit as shown in the figure is


$x \times 10^{-1}$ watt. The value of x , to the nearest integer, is ____ .



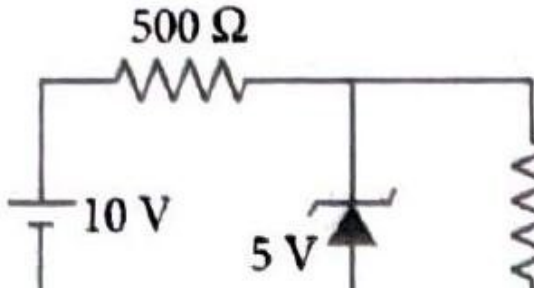
Q 43. In the following circuit, the current flowing through $1\text{k}\Omega$ resistor is ____ mA .



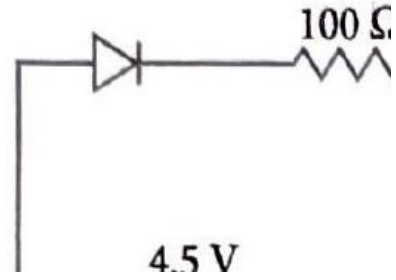Q 44. Figure shows a diode connected to an external resistance and an emf. Assuming that the barrier potential developed in the diode is 0.5 V , then the value of current (in mA) in the circuit is ____ .



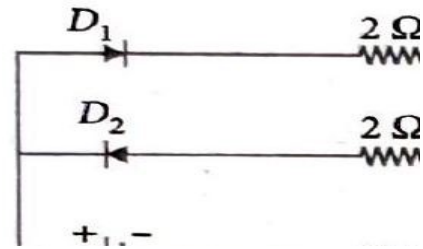Q 45. Assuming that the two diodes D_1 and D_2 used in the electric circuit shown in the figure are ideal, the value of the current (in A) flowing through 1Ω resistor is ____



ANSWER

Logic Gates

Straight Objective

Q 1.	d	Q 2.	d	Q 3.	d	Q 4.	b
Q 5.	c	Q 6.	b	Q 7.	d	Q 8.	d
Q 9.	b	Q 10.	d	Q 11.	b	Q 12.	c
Q 13.	a	Q 14.	a	Q 15.	d	Q 16.	c
Q 17.	a	Q 18.	a	Q 19.	b	Q 20.	b

Integer type

Q 21.		Q 22.		Q 23.		Q 24.	
Q 25.							

Zener Diode

Straight Objective

Q 26.		Q 27.		Q 28.		Q 29.	c
Q 30.		Q 31.		Q 32.		Q 33.	a
Q 34.	b	Q 35.		Q 36.	c	Q 37.	c
Q 38.	c	Q 39.	b	Q 40.	b		

Integer type

Q 41.		Q 42.		Q 43.		Q 44.	
Q 45.							